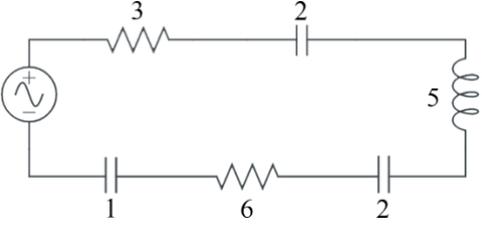
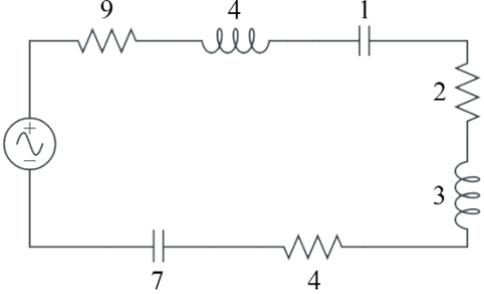


USER MANUAL—CALCULATIONS

Calculating Total Impedance

Use the circuit diagrams below to calculate the total impedance for each circuit. Write your final answer in standard form: $a + bi$.

Question 1	Question 2
	
<p>Total Impedance = _____</p>	<p>Total Impedance = _____</p>

Calculating Voltage

Voltage = (Current)(Impedance) is the formula that relates voltage, current, and total impedance. Use this formula in each of the following scenarios to calculate the voltage. Write your final answer in standard form: $a + bi$.

Question 3	Question 4
<p>What is the voltage in a circuit with current $7 + 5i$ and impedance $8 - 6i$?</p>	<p>What is the voltage in a circuit with current $5 + 8i$ and impedance $5 - 8i$?</p>
<p>Voltage = _____</p>	<p>Voltage = _____</p>

Calculating Current

Use the formula $\text{Voltage} = (\text{Current})(\text{Impedance})$ in each of the following scenarios to calculate the current. Write your final answer in standard form: $a + bi$.

Question 5

What is the current in a circuit with voltage $2i$ and impedance $1+i$?

Current = _____

Definition

- The **complex conjugate** of $a+bi$ is $a-bi$.
 - For example, $9+4i$ is the complex conjugate of $9-4i$.

Use the complex conjugate and the voltage formula (from above) to calculate the current. Write your final answer in standard form: $a + bi$.

Question 6

What is the current in a circuit with voltage $2+5i$ and impedance $5+2i$?

Current = _____